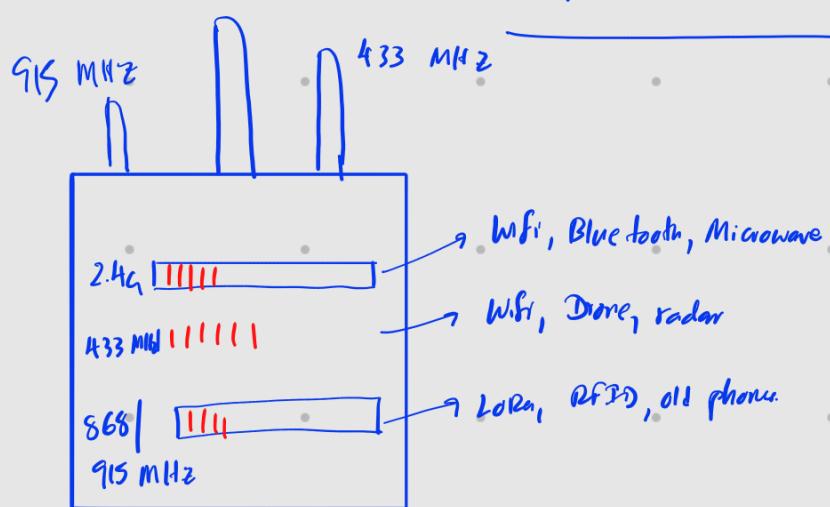



RF sniffer



Simple block diagram




For 1 band of RF sniffer

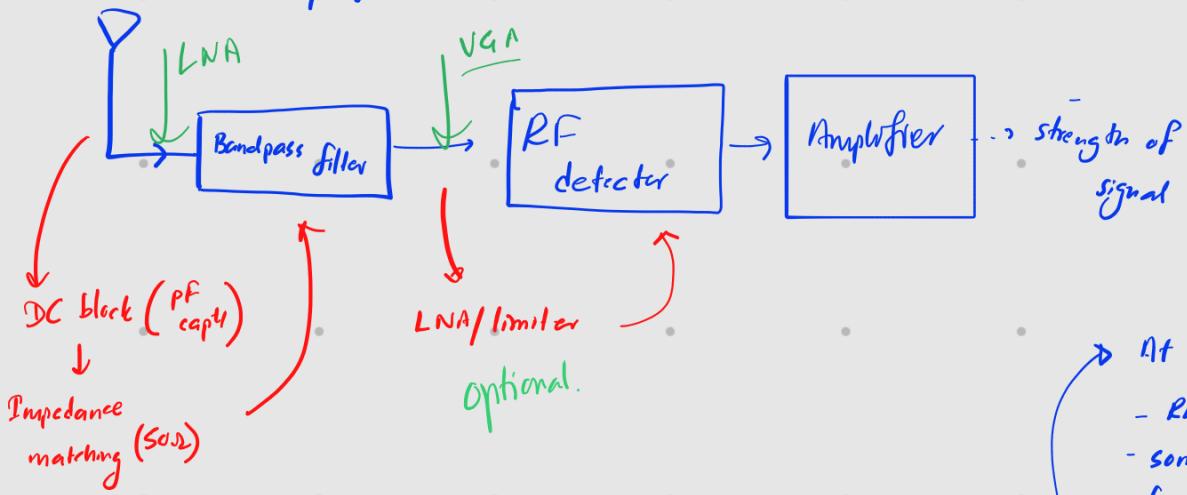

At GHz, MHz scale,
 - RLC parasitic
 - Some components' self resonance frequency (SRF)

Bandpass-filter

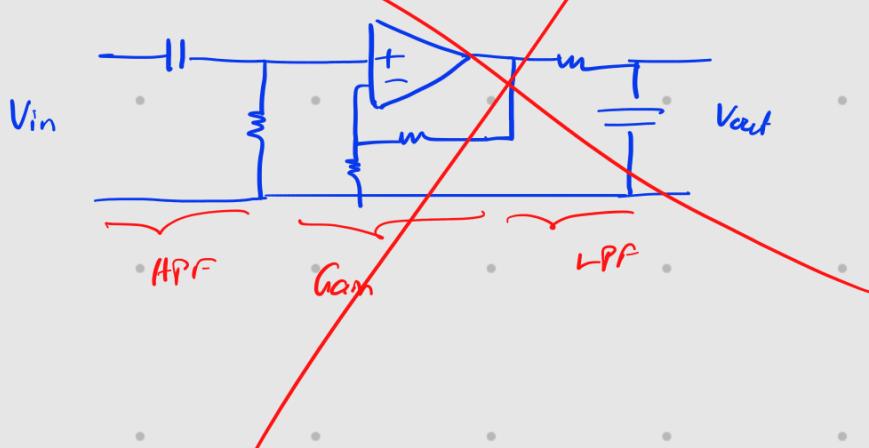① Combination of LPF and HPF (Active BPF)



Not possible
for GHz, MHz



Solu^m for BPF

- 1) SAW
- 2) microstrip
- 3) Cavity filter.

(2)

2.4 GHz

Normal RLC \rightarrow Heavy parasitic loss
 \rightarrow Low Q = Center frequency / Bandwidth


Active op-amp \rightarrow Can't give enough gain-bandwidth @ GHz
 \rightarrow RF op-amps - cost & noise add

~~SAW~~ \rightarrow Cost
 \rightarrow Fixed response with sharp skirts
 \rightarrow High insertion loss
 \rightarrow Best @ interference rejection

3 pole microstrip hairpin \rightarrow Not sharp as SAW
 \rightarrow Low noise & insertion loss

B7520 - Qualcomm

SAW filter for 2.4 GHz band

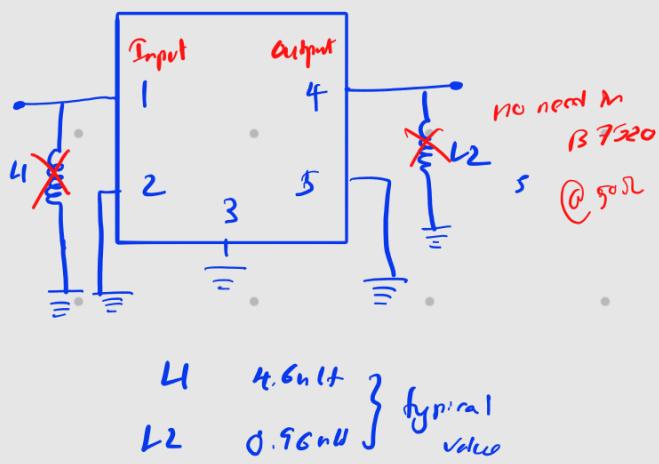

How does it work?

433 MHz


Microstrip hairpin \rightarrow Large PCB ($\approx 433 \text{ MHz}$)

~~SAW~~ \rightarrow Moderate insertion loss

3 pole LC } \rightarrow Best since supports high BW
 resonator ladder & steeper edges, expensive


LC ladder \rightarrow Captures whole 433MHz with less tuning

433GHz - SAW

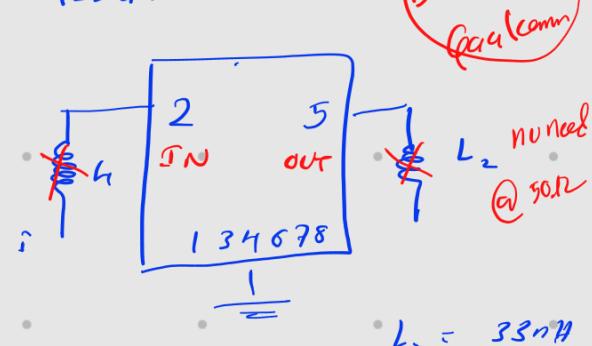


B3710
 Qualcomm

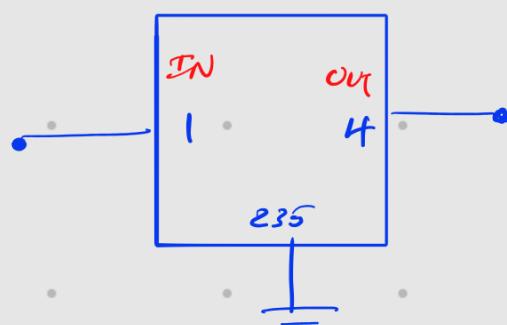
915MHz \rightarrow SAW \rightarrow Good Q factor




B3710
 Qualcomm

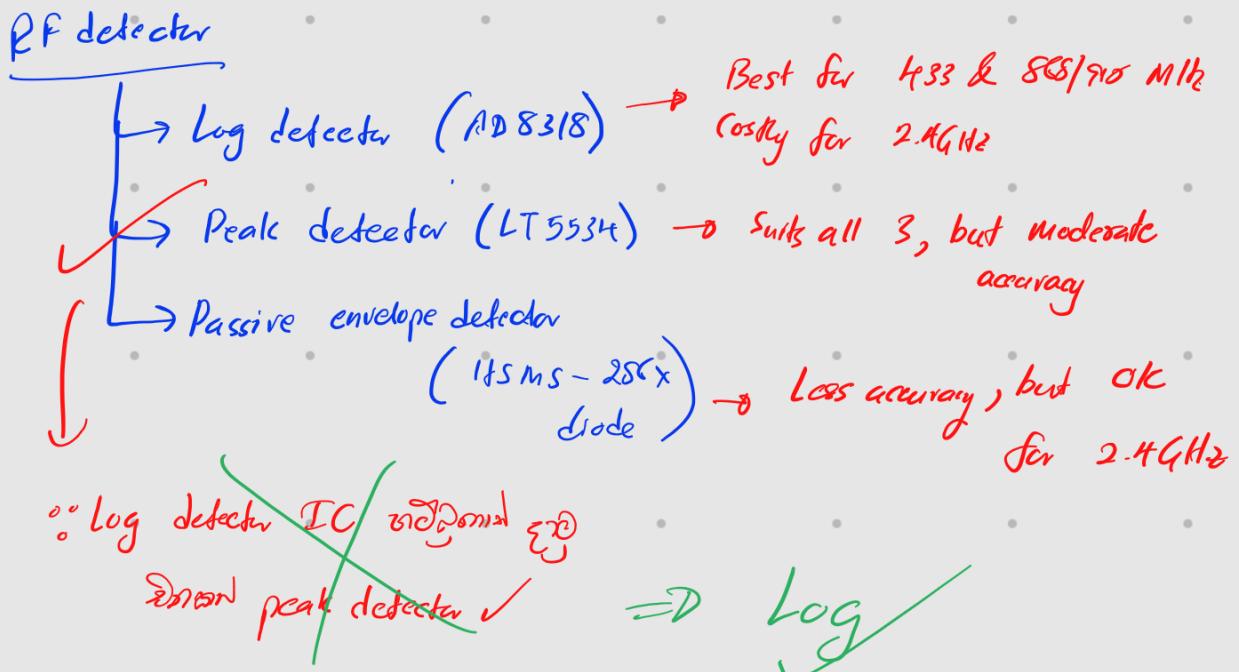

Log detector.

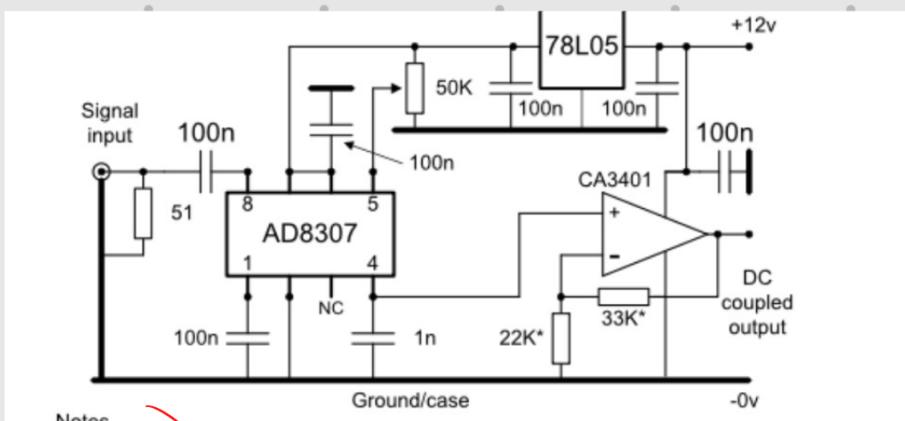

Peak detector

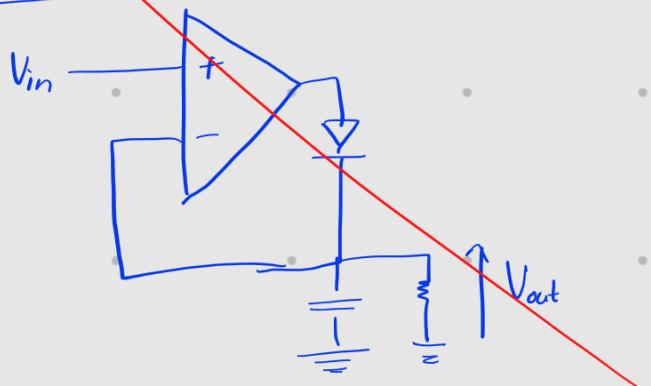


Level indicator

can use on

LED bargraph


RF detector
output

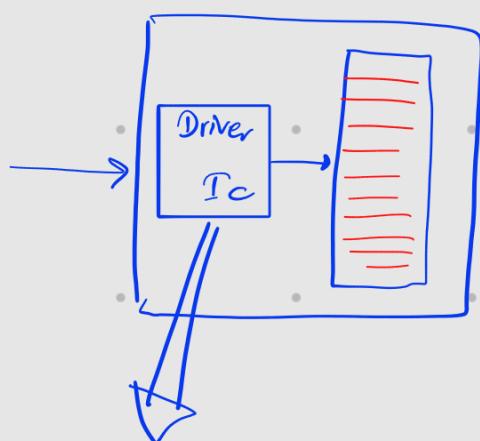

LM3914 — for linear voltage output.

✓ LM3915 — for log voltage outputs

Rough Schematic

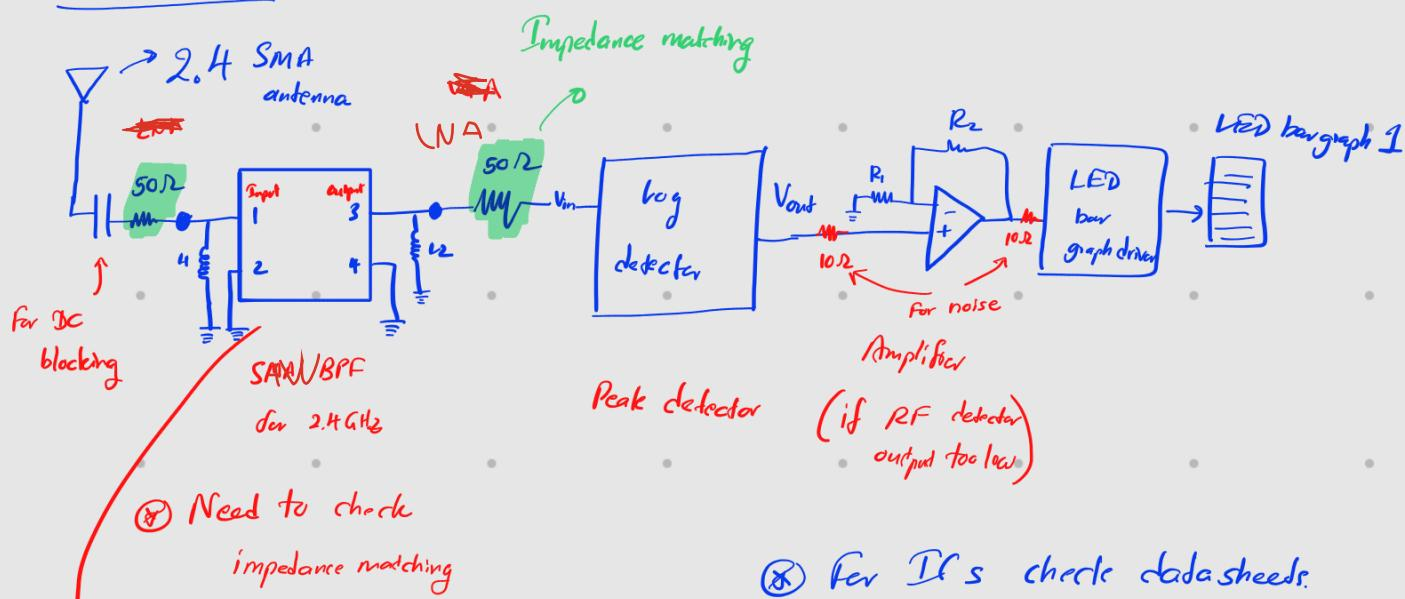

OR microstrip filter

log - AD3807

ANT -> FILTER -> LNA -> VGA -> ENVELOPE DETECTOR -> LM3914 -> LED

LG

H1

CD
TSR

Characteristics to consider in filter design

- 1) Cutoff frequency → For BPF lower & higher
- 2) Bandwidth
- 3) Pass band ripple → Variation in gain inside the passband
- 4) Stop band attenuation → How much unwanted frequencies are suppressed
- 5) Roll-off rate → Sharpness of transition.
- 6) Noise figure (NF)

④ In this context



Proposed design

mini zigzag ☺

PCB material - FR-4

$$\epsilon_r = 4.4$$


$$f_c = 2.45 \text{ GHz}$$

$$h = 1.6 \text{ mm}$$

$$FBW = 5\%$$

50Ω → 3.08mm width

Resonator line → 1.24mm (80Ω)

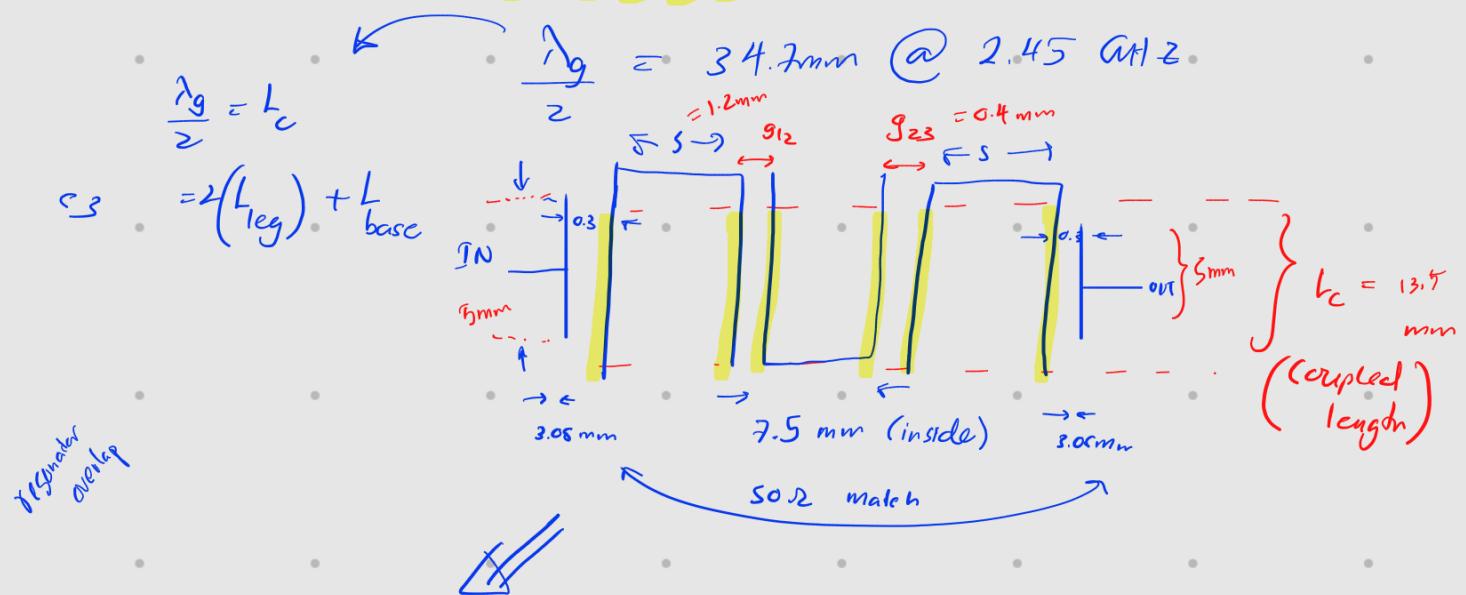

lowpass (lumped module) parameters

$$g_0 = 1 = g_4$$

$$g_1 = 1.5963 = g_3$$

$$g_2 = 1.0967$$

$$\Phi_{e1} = \Phi_{e3} = 26.6$$

$$M_{12} = \frac{FBW}{\sqrt{g_1 g_2}} \approx 0.046$$

$$M_{23} \approx 0.046$$

Chebyshev table ($n=3$)

$$g_0 = 1.0316 = g_4$$

$$g_1 = 1.1474 = g_3$$

Possible ρ^{air}

1) Why PCB filter? \rightarrow low insertion noise
 \rightarrow To leave $\otimes\otimes$

2) Why hairpin? \rightarrow less area
 \rightarrow narrowband friendly

3) Why 3-pole hairpin?
 \rightarrow For higher orders more parasitic effect

